
Lab (4) TDR

MTLINE Settings

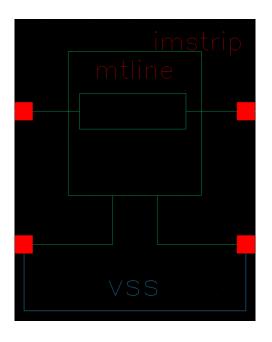

Line_length = 0.15

Dielectric_const = 4.8 Dielectric_thickness = 360u Line_width = 625um Line_thickness = 17.78u → For 1ns travel time in transmission line (2ns back & forth)

For Zo = 50 Ohms

Mtline:

Library Name	analogLib					
Cell Name	mtline					
View Name	symbol					
Instance Name	imstrip					
CDF Parameter	Value					
Num of lines (excluding	ref 1					
Model name						
Physical length	line_length M					
Multiplicity factor	1					
Max signal frequency	_					
Type of Input	FieldSolver -					
Generate noise?	no 🔽					
Transmission line type	microstrip 🔽					
Model type	wideband 🔽					
Rel dielectic const of	laye dielectric_const					
Dielectric layer thickness dielectric_thickness						
Signal line width	line_width					
Signal line thickness	line_thickness					
Signal line spacing						
Gnd Plane thickness						
Ground plane conductivi	ty					
Signal line conductivit	у					
Display	Cross-section					

Relationship between Length of transmission line & time taken for pulse to travel in the transmission line

$$Velocity(v) = \frac{Distance}{Time}$$


$$t_{reflection} = 2.t_{line}$$

$$= \frac{2L}{v} = \frac{2L}{c_{/\sqrt{\epsilon_r}}}$$

For
$$t_{line} = 1ns$$
:
$$L = t_{line} \cdot {^C}/{\sqrt{\epsilon_r}}$$


$$= 10^{-9} \cdot {^3x} \cdot {^{10^8}}/{\sqrt{4.8}}$$

$$L = 0.15 m$$

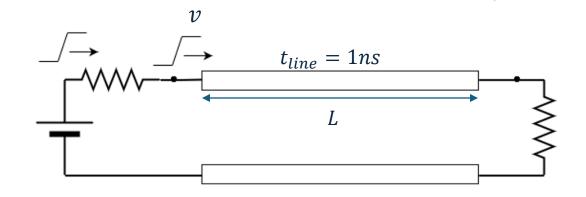


(A) Resistive Loads


TB1: Transient

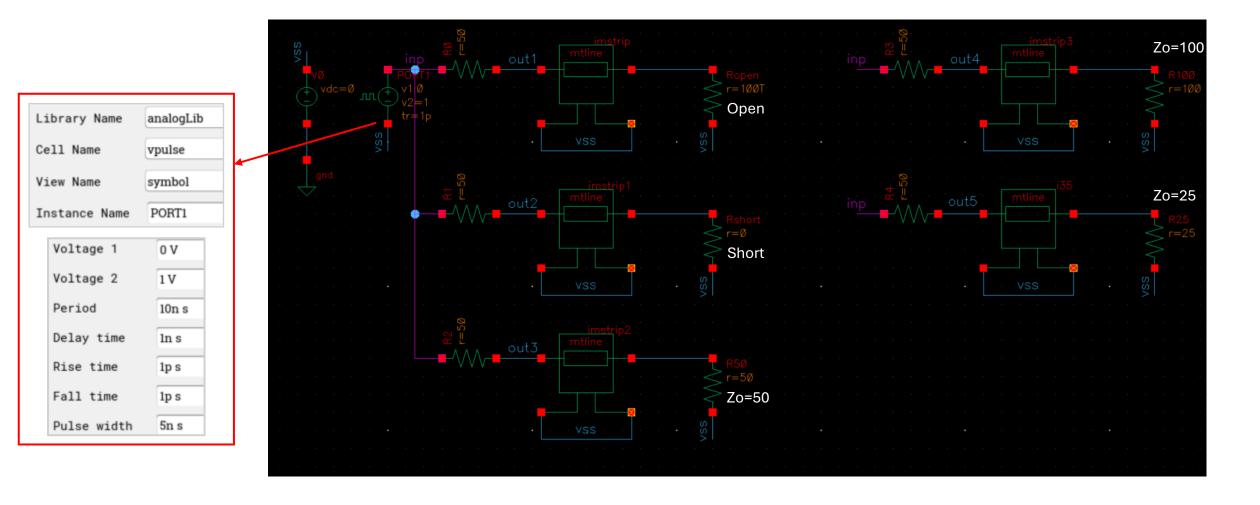


TB2: S-Parameters

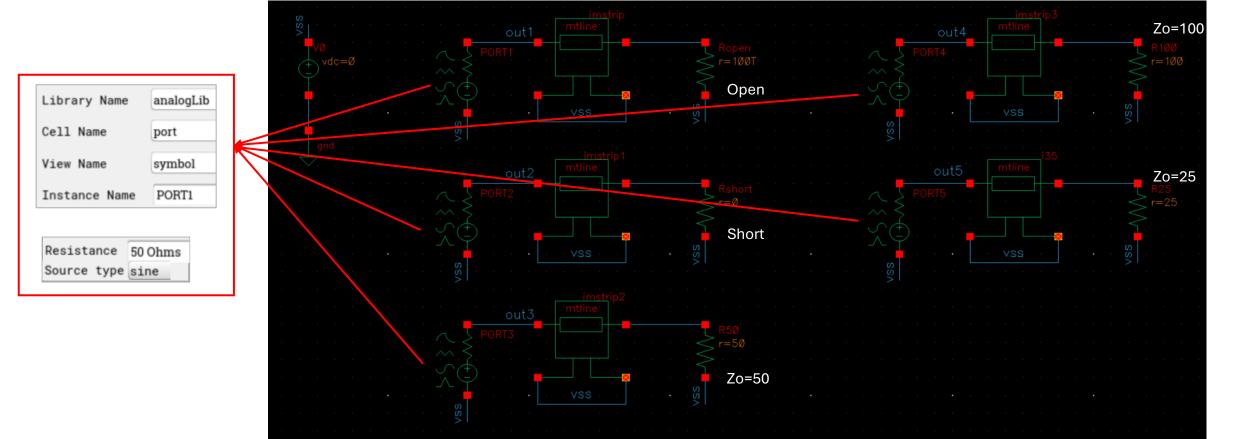



Analyses Setups

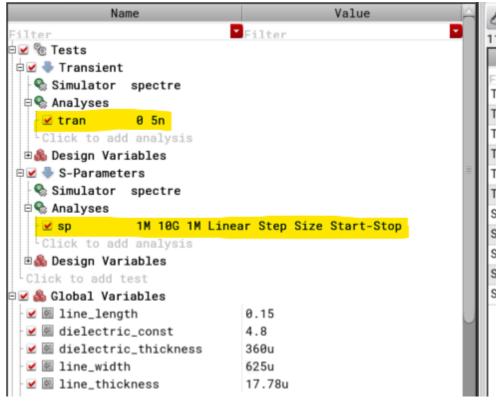



Test	Name	Туре	Details	EvalType	Plot
ilter	Filter Y	Filter Y	Filter	Filter	v
Transient		signal	/inp	point	✓
Transient		signal	/out1	point	✓
Transient		signal	/out2	point	✓
Transient		signal	/out3	point	✓
Transient		signal	/out4	point	✓
Transient		signal	/out5	point	✓
S-Parameters	S11 dB20	expr	db(spm('sp 1 1))	point	✓
S-Parameters	S22 dB20	expr	db(spm('sp 2 2))	point	✓
S-Parameters	S33 dB20	expr	db(spm('sp 3 3))	point	✓
S-Parameters	S44 dB20	expr	db(spm('sp 4 4))	point	✓
S-Parameters	S55 dB20	expr	db(spm('sp 5 5))	point	V

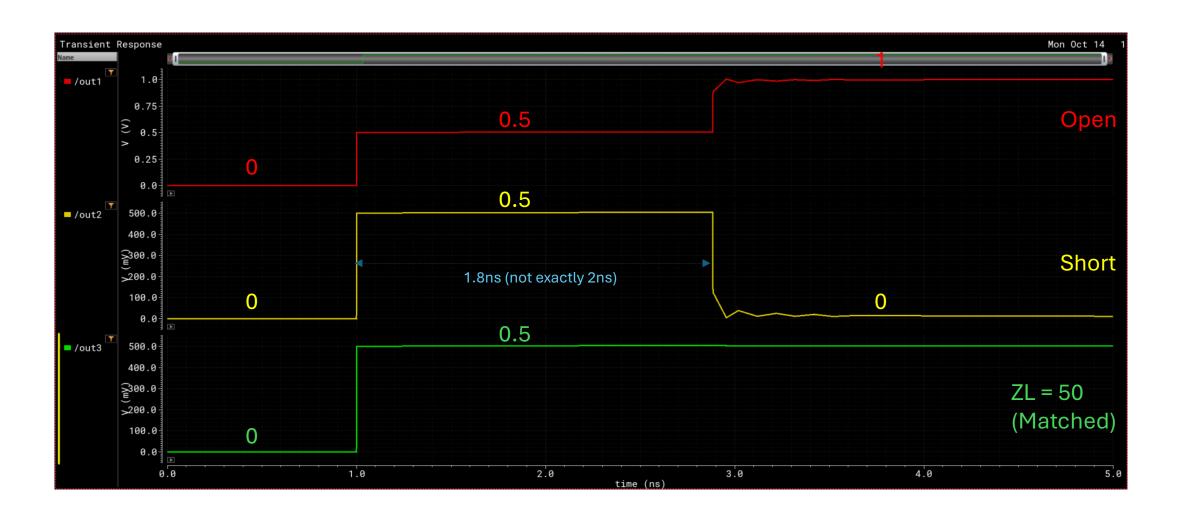

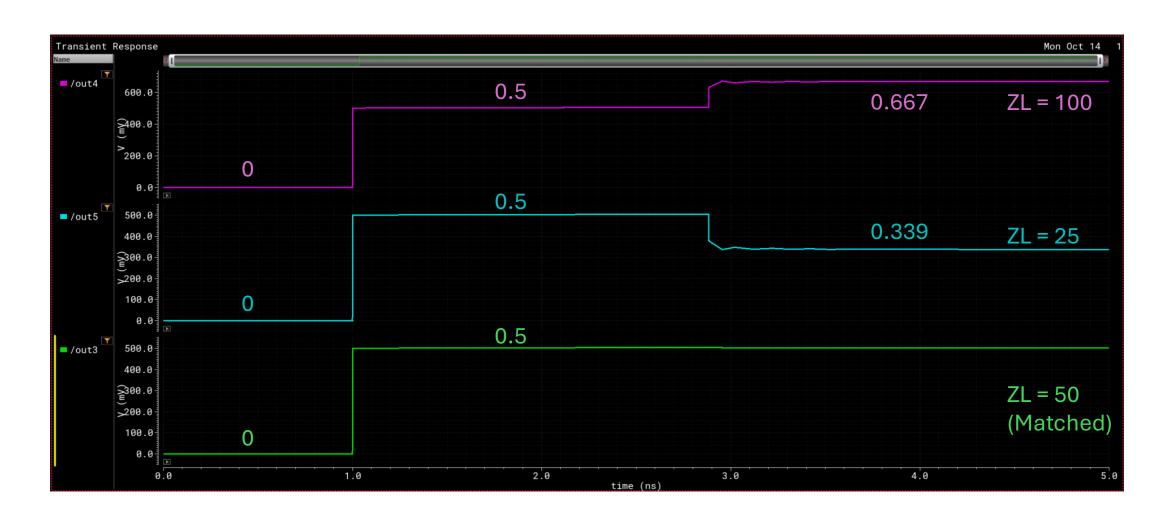

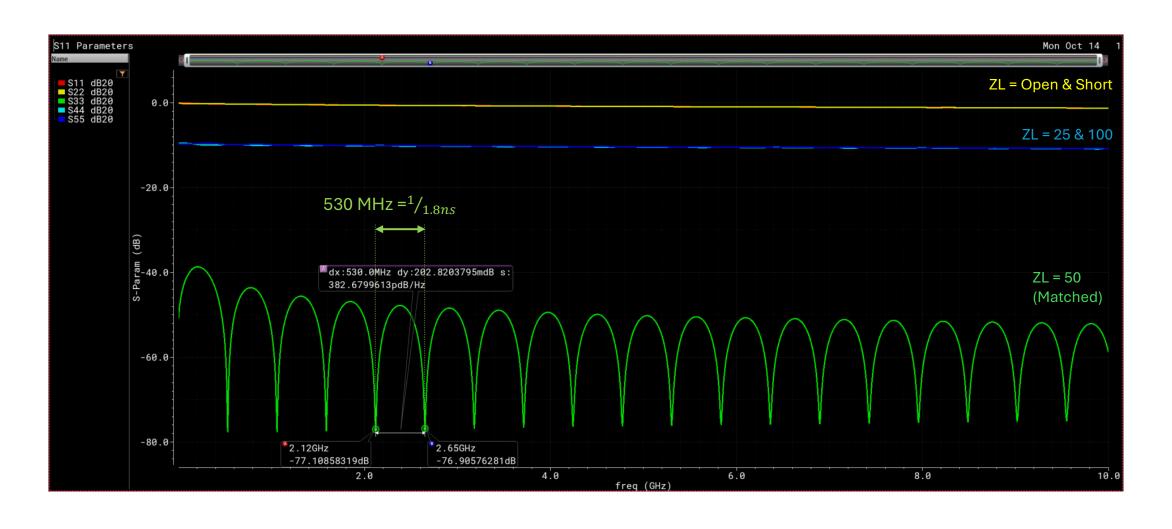


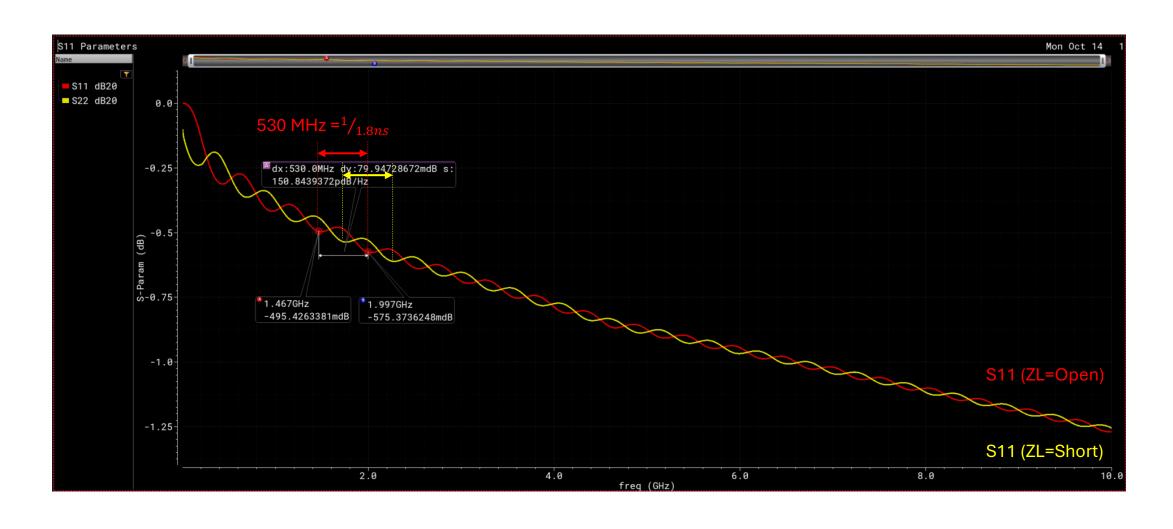

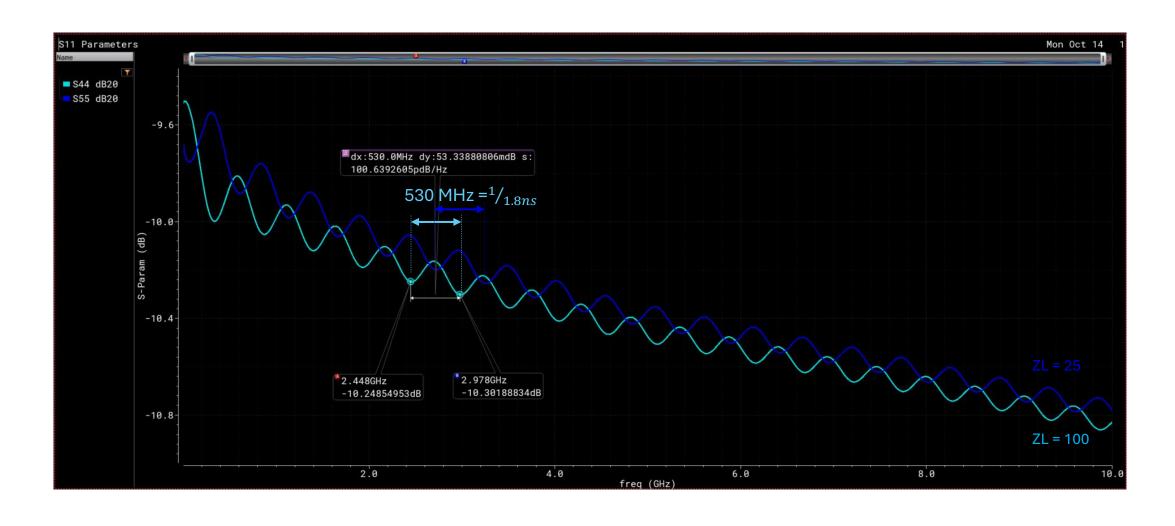


(B) Inductive & Capacitive Loads


TB1: Transient

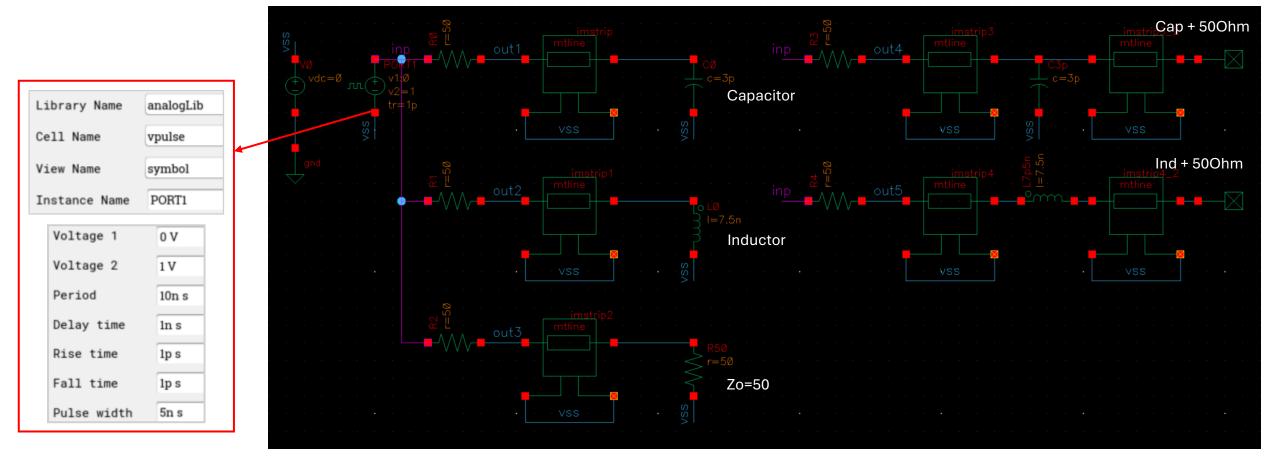


TB2: S-Parameters

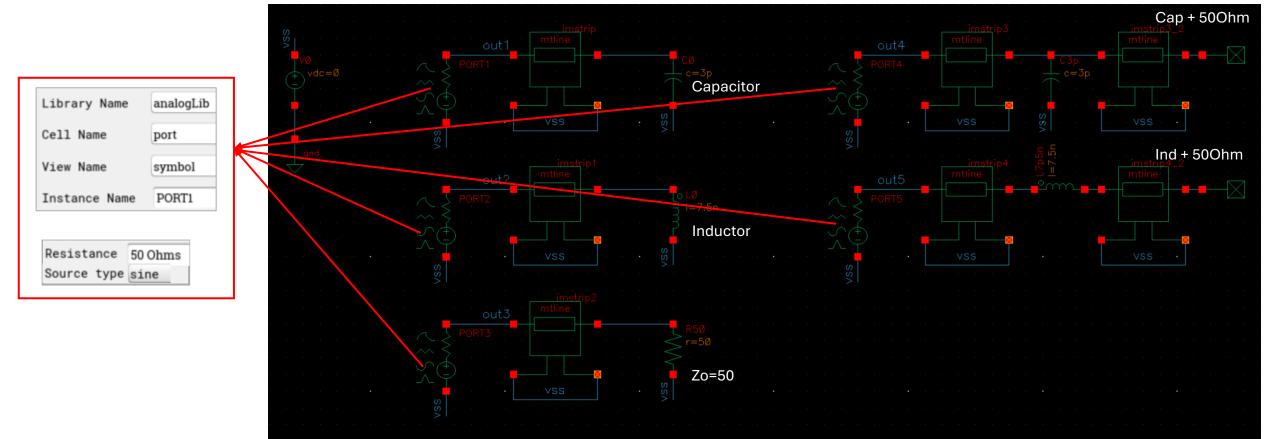



Analyses Setups

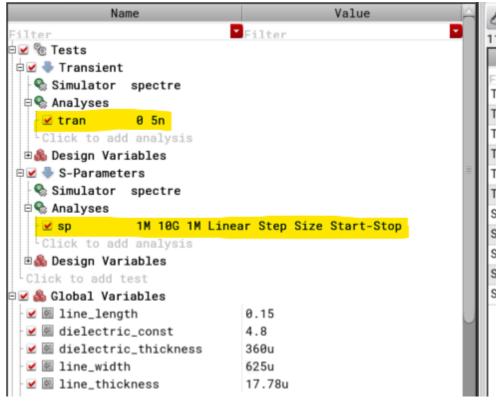



Test	Name	Туре	Details	EvalType	Plot
ilter	Filter Y	Filter Y	Filter	Filter	v
Transient		signal	/inp	point	✓
Transient		signal	/out1	point	✓
Transient		signal	/out2	point	✓
Transient		signal	/out3	point	✓
Transient		signal	/out4	point	✓
Transient		signal	/out5	point	✓
S-Parameters	S11 dB20	expr	db(spm('sp 1 1))	point	✓
S-Parameters	S22 dB20	expr	db(spm('sp 2 2))	point	✓
S-Parameters	S33 dB20	expr	db(spm('sp 3 3))	point	✓
S-Parameters	S44 dB20	expr	db(spm('sp 4 4))	point	✓
S-Parameters	S55 dB20	expr	db(spm('sp 5 5))	point	V

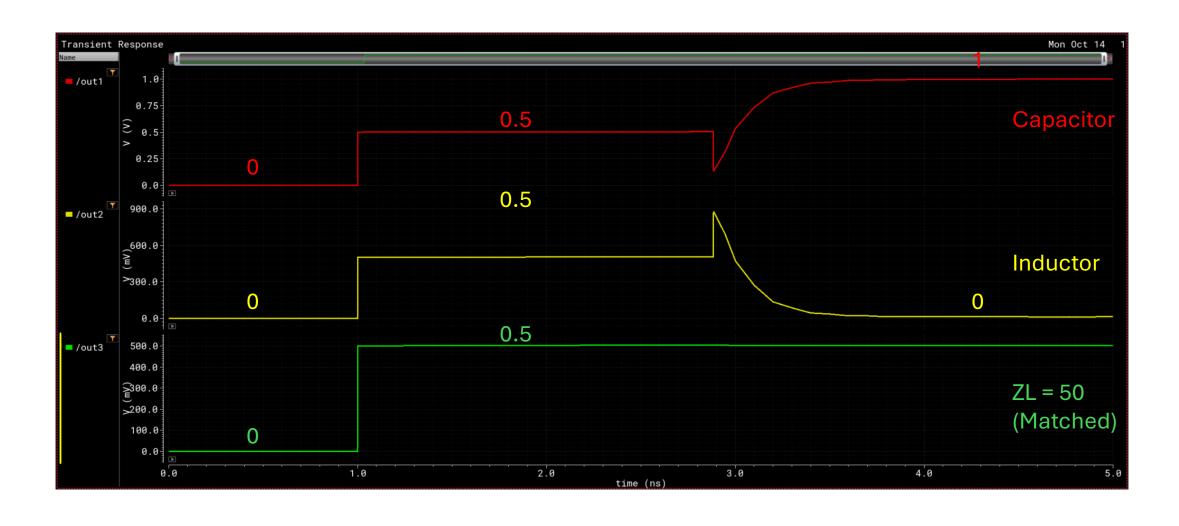

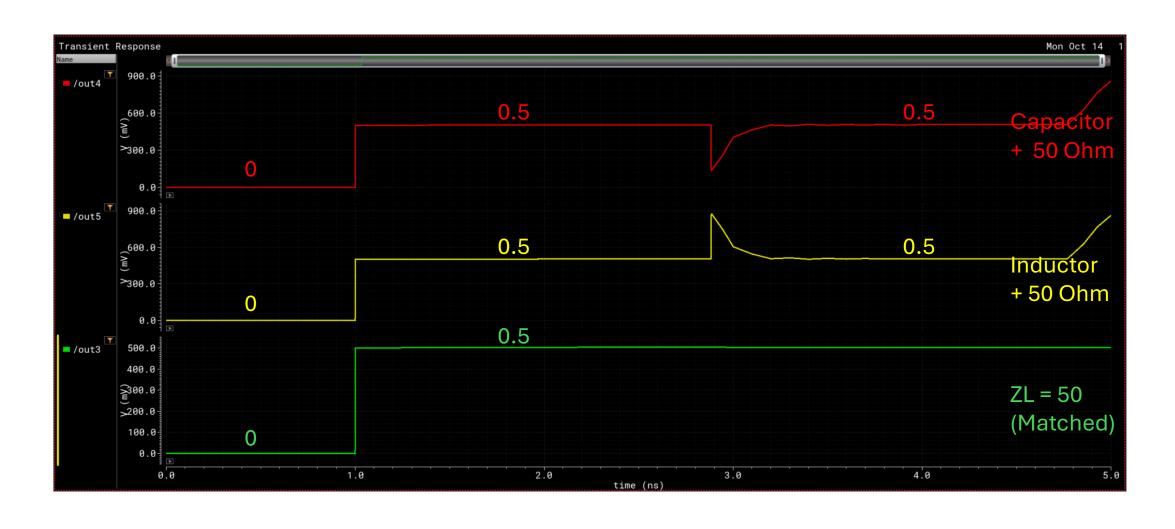

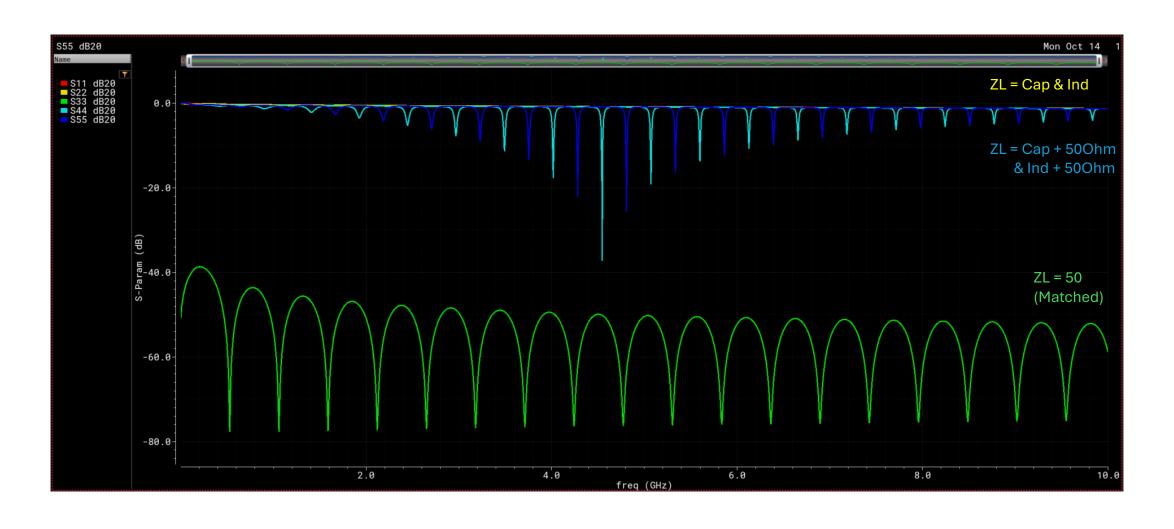

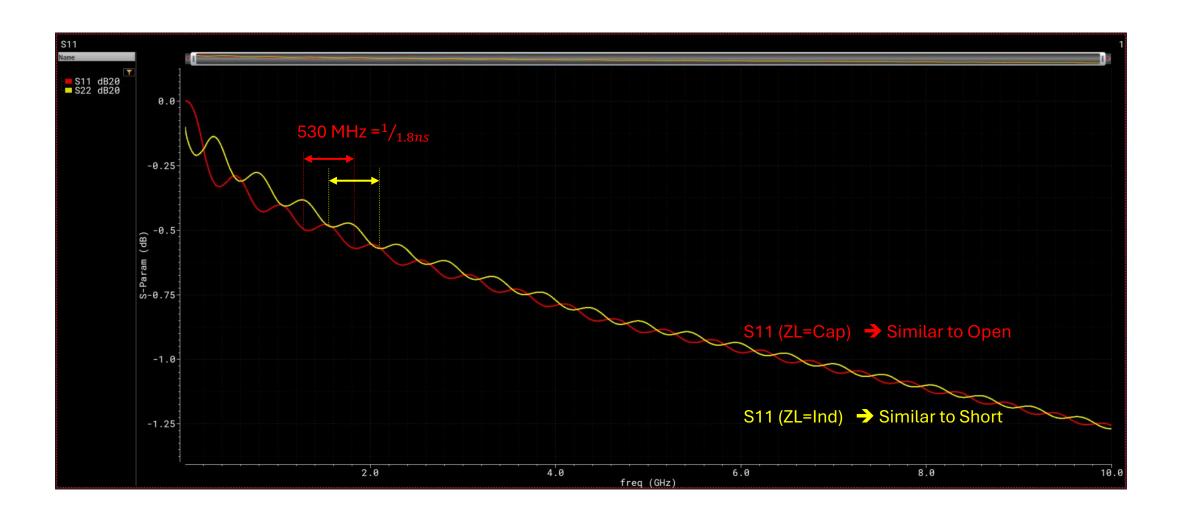


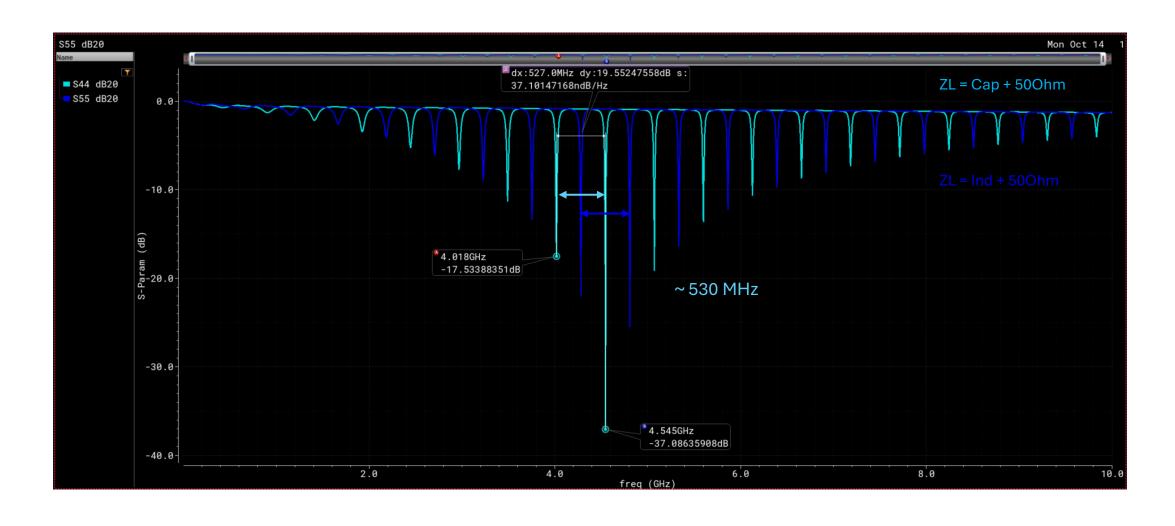


(C) LC Network Loads


[1] Series LC network


TB1: Transient

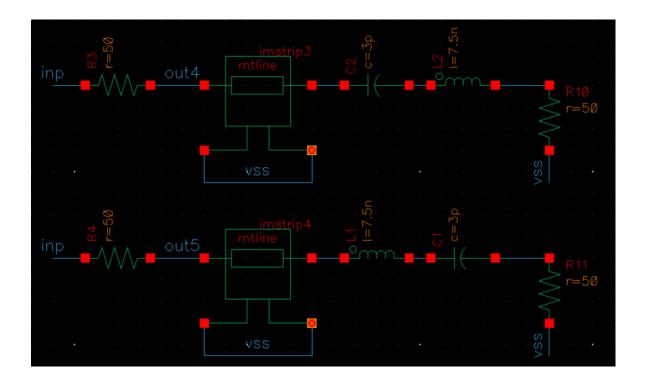

TB2: S-Parameters

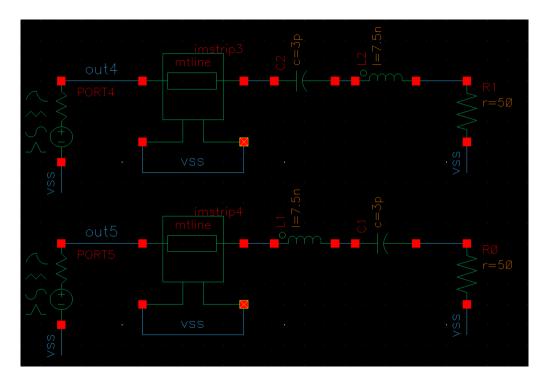


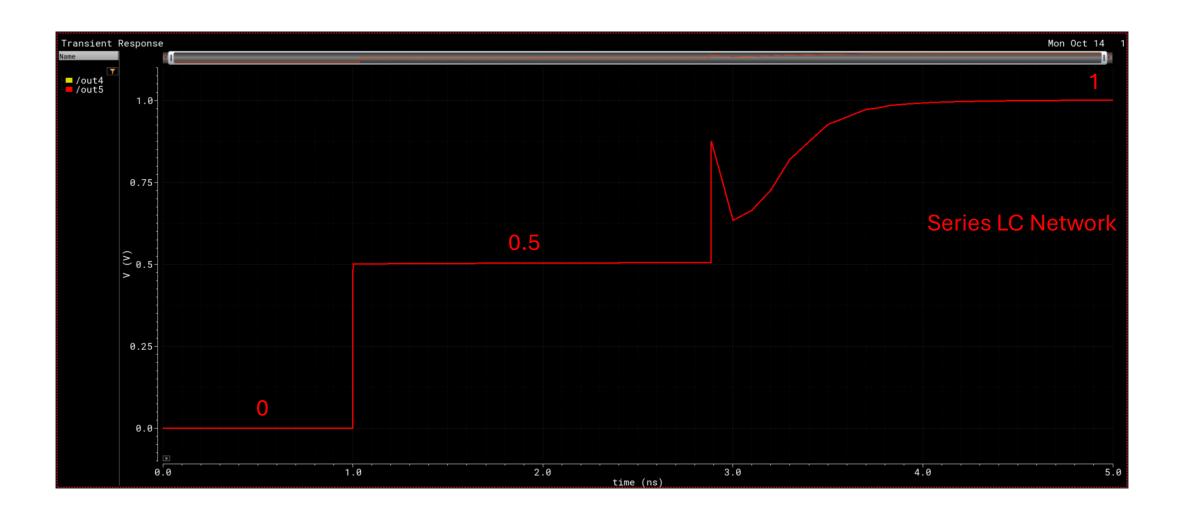

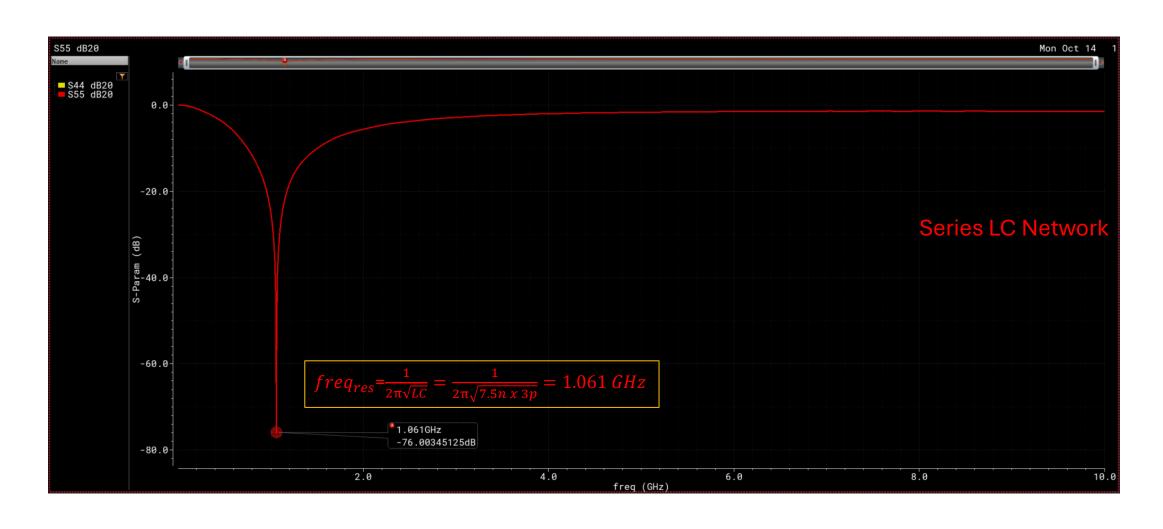

[2] Parallel LC network

TB1: Transient

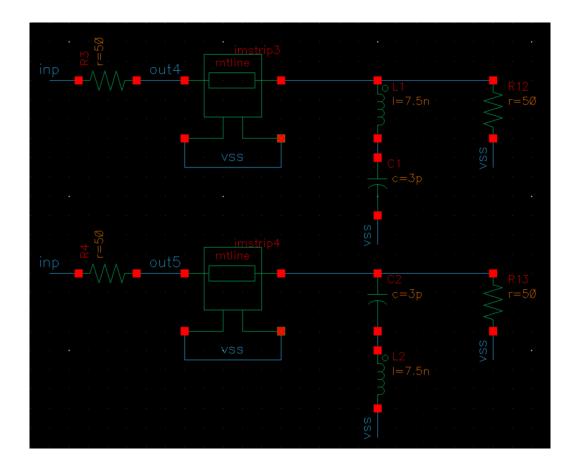

TB2: S-Parameters

